

Advanced Architecture Lab-3

Briefing

School of Electrical Engineering
Faculty of Engineering
Tel Aviv University


Verilog

- The HDL we will use in our lab is **Verilog**
- Verilog's capabilities:
 - **Design and Verification of digital circuits**
 - Verification of mixed-signal or analog circuits
- Established in 1984; kept proprietary until 1991;
 - 1995: Verilog-95: first IEEE-standardized version!
 - **2001: Verilog-2001: significantly upgraded! ← We use this**
 - 2005: Verilog-2005: insignificant upgrades
 - 2009: Verilog was merged into SystemVerilog
- <http://www.asic-world.com/verilog> is the best guide

Verilog is not a programming language

- It is a hardware description language
- The code describes an underlying circuit
- All the code is **continuously active in parallel**, not like C which is sequential
- Verilog syntax is very similar to the C syntax

Design Flow

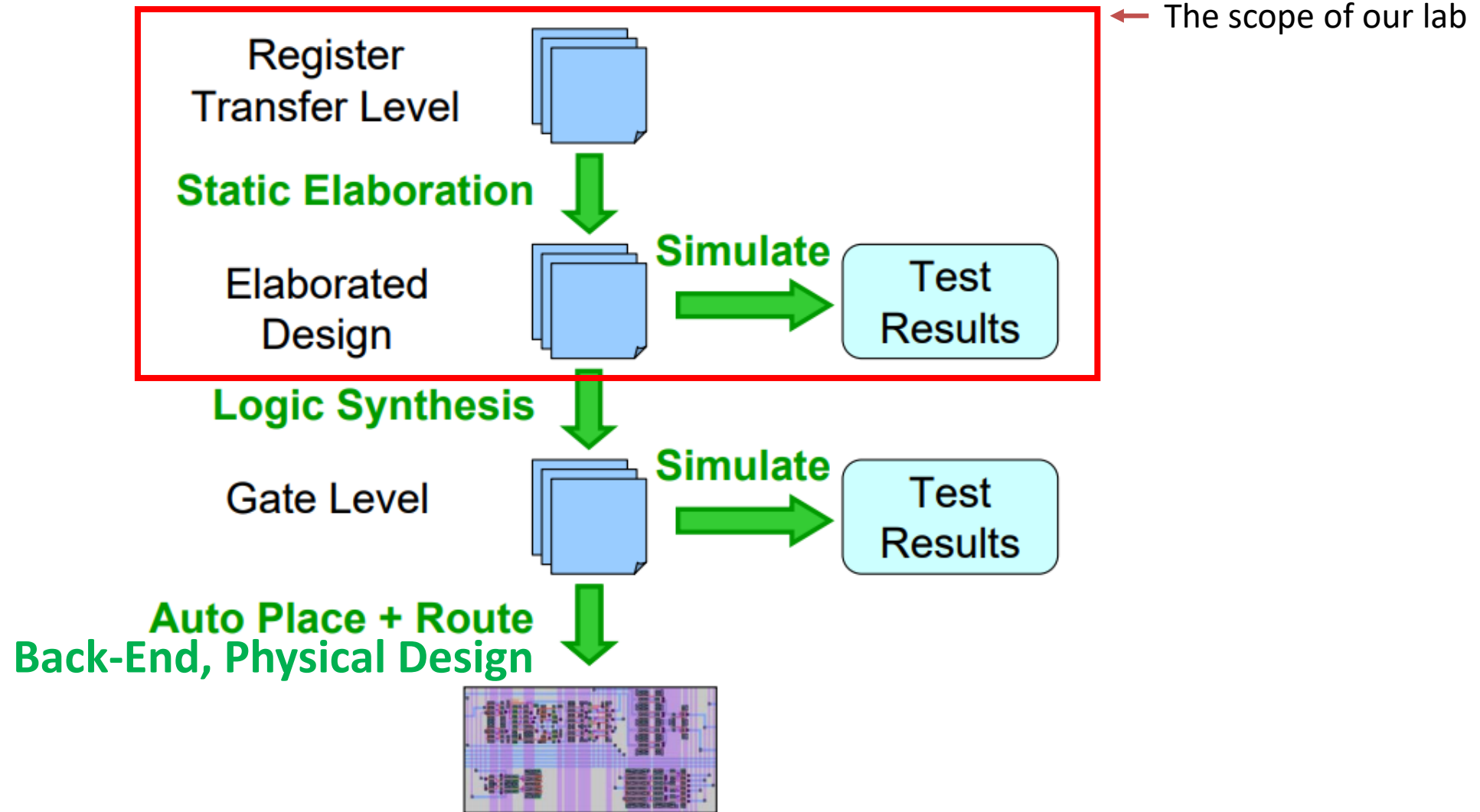

Hardware Data types

- **Single Bit:**

`reg r1` – `r1` keeps a value, which can be changed on another assignment
`wire w1` – `w1` is a net, which must be constantly driven by a signal

- **Busses and multiple bit registers** (MSB is on the left, unsigned by default)

`reg [3:0] r1`
`wire [3:0] w1`

- **Signed busses and multiple bit registers** (two's complement)

`reg signed [3:0] r1`
`wire signed [3:0] w1`

Virtual Data types

`integer` – 32-bit two's complement integer value

`real` – 64-bit (double precision) IEEE floating point value

`realtime` – used for storing time as floating point


`time` – 64 bit unsigned value for the simulation time counting

`genvar` - positive integer values. The index variable used in a `generate` loop must be declared as a `genvar`

Operators

- Reduction means “tree”:
 - $\wedge A[2:0]$ is a xor-tree of 3 bits - returns 1 bit, equivalent to $A[2] \wedge A[1] \wedge A[0]$ and to $\wedge \{A[2], A[1], A[0]\}$
- Bitwise:
 - $A \& B$ performs bitwise and between buses A and B
- Logical
 - $A == B \&\& B == C$ returns only one bit!
- Arithmetic
 - $A >>> 3$ is arithmetic right shift of A by 3 bits
 - Comparison $A < B$ respects whether A and B are signed.
- Concatenation operator

$w1 = \{r1[1:0], r1[3:2]\};$

 

!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic
<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	case equality	equality
!=	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional “ternary if-the-else”	conditional

Signal values

- single bit values: **0, 1, Z, X**
- multiple bits : use the pattern [Width]'[Radix][Value]
 - For example: 4 'b1100
 - Number of bits binary fill the string 1100
- Other available radices 'h' 'd' for hexadecimal and decimal
- The bit width of the value must match the width of the wire/reg
- Default representation radix is decimal:
 - Example: all following unsigned numbers are equal:
 - Example: all following signed numbers are equal:

X=12;	X=4'hc;	X=4'b1100;	X=4'd12;
X=-1;	X=4'hf;	X=4'b1111;	X=-4'd1;
	X=-4'h1	X=-4'b0001	

Module Definition

- Module describes a synchronous/combinational circuit
- Good practice: write each module in its own .v source file
- There must be one **top module** that interfaces with the external system

```
module Fifo(in,push,out);  
    parameter N=2;  
    input in;  
    input push;  
    output out;  
    //some logic goes here  
endmodule
```

Parameters: are set once per module instance, they are not changed during operation as opposed to inputs/outputs

Input/Output ports: are ports through which the signals are fed in/out of the module.

Module Instantiation

- Design hierarchy is constructed by instantiating modules in other modules
- An instance of a module is a use of this module in another, higher-level module
- **Single instance:**


```
reg in, push;  
wire out;  
Fifo #(4) myFifo(in, push, out);
```

Module name

Param.

Instance name


Wirings

 

Module Instantiation

- Array of instances
 
```
reg [3:0] in;  
reg push;  
wire [3:0] out;  
Fifo fifoArr[3:0](in, {4*{push}}, out);
```




Generate block

```
reg [3:0] in;  
reg push;  
wire [3:0] out;  
genvar i;  
generate  
  for ( i = 0; i < 4; i = i+1 )  
    begin : fifoArr  
      Fifo f(in[i], push, out[i]);  
    end  
endgenerate
```

genvar is a datatype used for the generate block indexing (virtual). It is not part of the circuit.

 generate syntax enables usage of **loops**, **if-else**, **case**




Static elaboration

- The following features of Verilog are “virtual” and are used only during static elaboration:
 1. Parameters
 2. Generate blocks
 3. Genvars

Conditional Hierarchy Construction

```
module Dual_Fifo(in, left, left_out, right_out);  
    parameter N=4;  
    input in;  
    input left;  
    output left_out;  
    output right_out;  
    generate  
        if (N == 1) begin  
            Fifo #(1) rightFifo(in, ~left, right_out);  
            Fifo #(1) leftFifo(in, left, left_out);  
        end else begin  
            Fifo #(N/2) rightFifo(in, ~left, right_out);  
            Fifo #(N/2) leftFifo(in, left, left_out);  
        end  
    endgenerate  
endmodule
```

 

Pay attention:

- Only **generate** allows a conditioned instantiation (i.e. if-else, loops, cases).
- `in`, `left`, `left_out`, `right_out` are **wires** by default, act as internal signals of the `Dual_Fifo`
- More **wires/regs** can be defined for internal usage within the `Dual_Fifo` module.
- Specifying a wire in multiple terminals – effectively short-circuits these terminals (see the `in` wire)

Combinational logic

- Continuous assignment

```
assign result_w = (select) ? b : a;
```

Every destination of continuous assignment must be declared as **wire**

- Behavioral always@ block

```
always @(a or b or select)
begin
    if (select == 1)
        result_r = b;
    else
        result_r = a;
end
```

Sensitivity list: the always@ block will be triggered only when these signals change

In combinational logic “always @” statements, you must not leave if statements without else as well as you must not leave switch statements without a default. Otherwise, a **latch will be inferred** in order to keep the previous value of “result”. An inferred latch is a common design mistake.

Every destination of always block must be declared as **reg**, however it won't be necessarily synthesized into a register hardware.

Combinational logic summary

- **assign** (single liner) describes signal assignments to a **wire** element
- Tip: use **assign w1**=“some important Boolean expression” and then use w1 as a predicate in other places in your code.
- **always@** (block) describes signal assignments to **reg** element(s)
- Don't write **assign** inside an **always@** block, only outside the block
- In combinational logic:
 - never leave an **if** without **else**
 - never leave a **case** without **default**


Synchronous Logic Example: 32 shift registers

```
input reset, shift, clk;
input [31:0] in;
output [31:0] out;
reg [31:0] r1;
reg [31:0] r2;
reg [31:0] r3;

always@(posedge clk) begin
    if (reset) begin
        r1 <= 0; r2 <= 32'b0; r3 <= 32'h0;
    end else if (shift)
        begin
            r1 <= in;
            r2 <= r1;
            r3 <= r2;
        end
end
assign out = r3;
```

Important to notice:

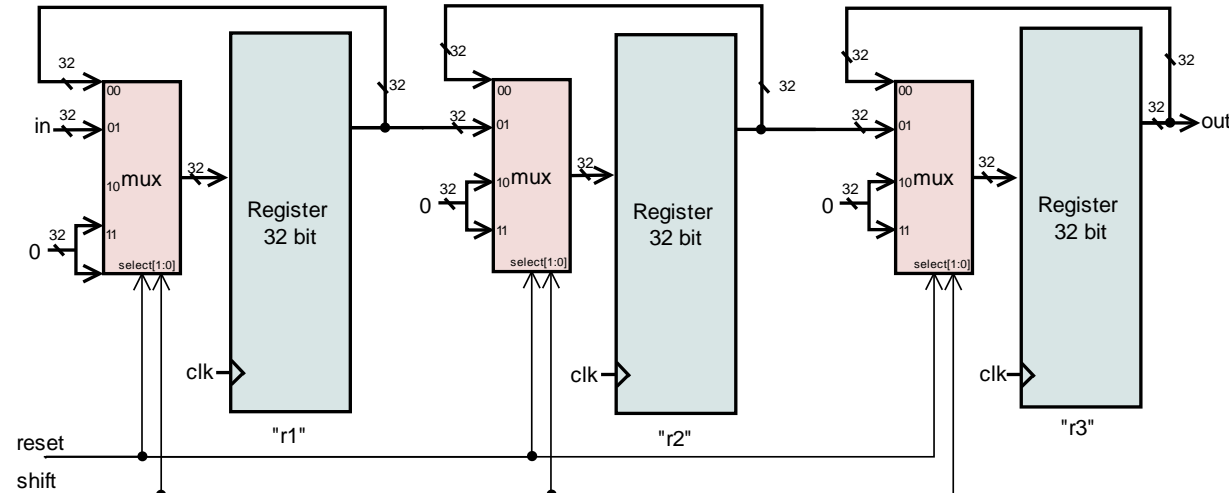- **posedge** is a saved word
- **Reset** is the only way to initialize the registers!
- **Make sure to have all registers initialized!**
- Use **<=** for proper flip flop assignment.
- All **<=** assignments are parallel, although written sequentially



Synchronous Logic – Blocking vs Non Blocking

```
module blocking (clk,a,c);  
    input clk,a;  
    output c;  
    reg c,b;  
  
    always @ (posedge clk)  
    begin  
        b = a;  
        c = b;  
    end  
  
endmodule
```

Simple Thumb rule:

- In combinational-logic
always@(*)

use =


- In synchronous-logic
always @(posedge clk)

use <=


sequential
"execution"
of code

parallel
"execution"
of code
 
```
module nonblocking (clk,a,c);  
    input clk,a;  
    output c;  
    reg c,b;  
  
    always @ (posedge clk)  
    begin  
        b <= a;  
        c <= b;  
    end  
  
endmodule
```




Synthesized products

 

Synchronous Logic – Reset


- Synchronous
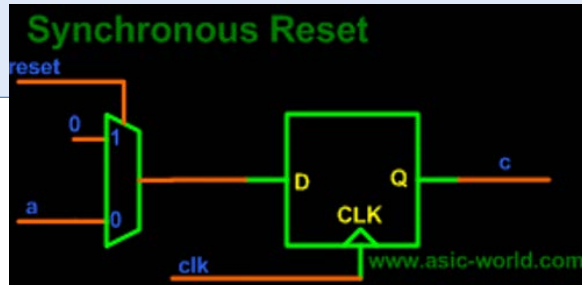
```
always @(posedge clk)
begin
if(reset == 1)
    begin
        //initializations
    end
else
    begin
        //actual stuff
    end
end
```




- Asynchronous
 
```
always @(posedge clk, posedge reset)
begin
if(reset == 1)
    begin
        //initializations
    end
else
    begin
        //actual stuff
    end
end
```




Synchronous Logic – State Machines

 - Example: **Arbiter(N)** is a circuit that helps resolving multiple requests to a shared resource. Arbiter(2) of 2 requestors can be implemented as a state machine with 2 inputs and 2 outputs, with a following functionality:
 - When req_0 is asserted, gnt_0 is outputted
 - When req_1 is asserted, gnt_1 is outputted
 - When both req_0 and req_1 are asserted then gnt_0 is asserted.
i.e. higher priority is given to req_0.
 - After one of the grant signals was asserted, its owner needs to go low to allow next arbitration.



Arbiter(2) schematic

 

Synchronous Logic – State Machines



```
module Arbiter (clk,reset,req_0,req_1,gnt_0,gnt_1);
    input  clk,reset,req_0,req_1;
    output gnt_0,gnt_1;

    localparam SIZE = 3;
    localparam IDLE = 3'b001,GNT0 = 3'b010,GNT1 = 3'b100 ;
    reg [SIZE-1:0] state;// Internal state

    //----- Transition function -----//
    always @ (posedge clk)
    begin
        if (reset == 1'b1)
            state <= IDLE;
        else
            case(state)
                IDLE :      if (req_0 == 1'b1)
                                state <= GNT0;
                            else if (req_1 == 1'b1)
                                state <= GNT1;
                            else
                                state <= IDLE;
                GNT0 :      if (req_0 == 1'b1)
                                state <= GNT0;
                            else
                                state <= IDLE;
                GNT1 :      if (req_1 == 1'b1)
                                state <= GNT1;
                            else
                                state <= IDLE;
                default :    state <= IDLE;
            endcase
    end

    //----- Output function -----//
    assign gnt_0 = (state == GNT0) ? 1 : 0;
    assign gnt_1 = (state == GNT1) ? 1 : 0;

endmodule
```

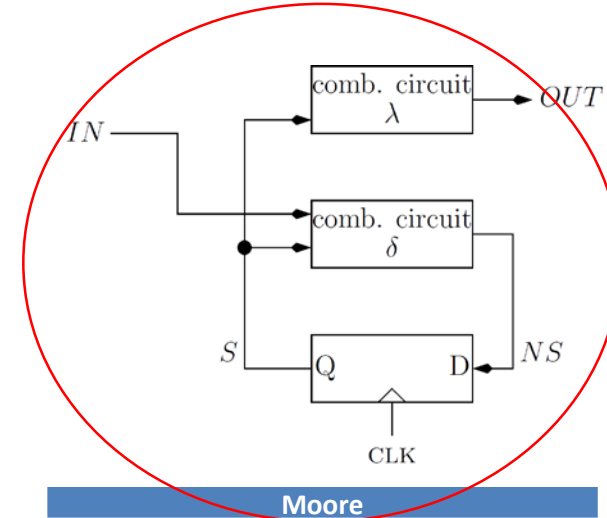 

Test Bench for Combinational Circuits

```
module FA_tb();
reg a, b, ci, correct, loop_skipped;
wire sum, co;
integer ai, bi, cii;
FA uut (a, b, ci, sum, co);
initial begin
correct = 1; loop_skipped = 1;
#1 for( ai=0; ai<=1; ai=ai+1 ) begin
  for( bi=0; bi<=1; bi=bi+1 ) begin
    for( cii=0; cii<=1; cii=cii+1 ) begin
      loop_skipped = 0;
      a = ai[0]; b = bi[0]; ci = cii[0];
      #5 correct = correct & (a + b + ci == {co,sum});
    end
  end
end
end
if (correct && ~loop_skipped)
  $display("Test Passed - %m");
else
  $display("Test Failed - %m");
$finish;
end
endmodule
```

- Integer data types, for loops, \$display and other "\$" functions are virtual creatures (not a part of the hardware).
- UUT/DUT is a generic name for Unit/Design Under Test instance
- initial - Same as always@ block, but performed only once
- initial - Could be thought of as a main() function
- initial - Useful in test benches
- Check the correctness against expected values. Don't just look at the waveform diagrams and say "seems fine to me".
- #5 creates a delay of 5 time units
- Print the test summary!


Delay notation must be either followed by a Verilog command or terminated by a semicolon ;

Test Bench for Synchronous Circuits

```
module Arbiter_tb();
reg clk, reset, req_0, req_1, correct;
wire gnt_0, gnt_1;
Arbiter uut (clk, reset, req_0, req_1, gnt_0, gnt_1);
initial begin
clk = 1; reset = 1; correct = 1; #1;
#20 reset = 0; req_0 = 1; req_1 = 0;
#10 correct = correct & (gnt_0 == 1 && gnt_1 == 0);
req_0 = 0; req_1 = 0;
#10 correct = correct & (gnt_0 == 0 && gnt_1 == 0);
req_0 = 0; req_1 = 1;
#10 correct = correct & (gnt_0 == 0 && gnt_1 == 1);
req_0 = 0; req_1 = 0;
#10 correct = correct & (gnt_0 == 0 && gnt_1 == 0);
req_0 = 1; req_1 = 1;
#10 correct = correct & (gnt_0 == 1 && gnt_1 == 0);
req_0 = 0; req_1 = 0;
#10 correct = correct & (gnt_0 == 0 && gnt_1 == 0);
#10 correct = correct & (gnt_0 == 0 && gnt_1 == 0);
if (correct==1)
$display("Test Passed");
else
$display("Test Failed");
$finish;
end
always #5 clk = ~clk;
endmodule
```

Tips:

 - Reset for a couple of cycles and create a 1ns shift after posedge
- Force test-inputs during the clock cycle for the to be sampled in the following posedge.
- Check the outputs of the current clock cycle



Timescale

- **`timescale 1 ns / 1 ps**
- In this example:
 - **1ns** is the basic time unit when using # (delay) notation. #10 will be equal to 10ns.
 - **1ps** is the resolution, which means that #(1.001) is the maximal precision you can use in the delay notation

Functions and Tasks

- **Function** cannot return more than one output, cannot contain delays, or call tasks. Can call other functions.
- Define

```
function myfunction;  
    input a, b, c, d;  
    begin  
        myfunction = ((a+b) + (c-d));  
    end  
endfunction
```

- Call

```
w1 = myfunction (a,b,c,d);
```

Notes:

- Use tasks and functions to write a particular code once and invoke it in many locations.
- Don't forget to specify input/output bit-width

- **Task** can drive many outputs, can call other functions and tasks
- Define

```
task convert;  
    input [7:0] temp_in;  
    output [7:0] temp_out;  
    begin  
        temp_out = (9/5) * ( temp_in + 32);  
    end  
endtask
```

- Call

```
convert (temp_a, temp_b);
```

Additional Important Lessons

- Apply Logic on data lines only. CLOCK or RESET gating must be done carefully to avoid glitches!
- Use `#10` (delays) and `initial` blocks only in test-benches! Not in the designs
- `reg` for output is a good practice - cuts the critical path, helps timing analysis. (Otherwise, the module fed by your module will extend the critical path)
- Every synchronous always block – must first reset ALL the registers if the reset is active. Otherwise: do all the logic.
- Don't use `initial` blocks for initialization

Running NCVERILOG

- `ncverilog +access+rw *.v`
 - Runs all the Verilog sources in the current directory. Performs the test benches.
- `simvision waves.vcd`
 - Opens a GUI, then choose signals and drag them right to the timeline view
- `/bin/tcsh`
 - If your shell doesn't recognize ncverilog