

Lab #3: Verilog introduction

In this lab we'll learn to use Verilog simulation tools using simple examples.

Technical notes:

A. In order to compile Verilog sources, use the following command within the directory that contains all the \*.v files:

```
ncverilog +access+rw *.v
```

B. In order to see the wave-diagram of the previous Verilog simulation use:

```
simvision waves.vcd
```

Assignments:

For each exercise, submit the verilog source files, a log of the testbench run, and a wave screenshot if requested.

1. Mux

The file mux.v contains two implementations of a 2:1 mux: the first using continuous assignment syntax, and the second using an always block. Both have the following inputs/output:

```
module mux1(a,b,select,result);
    input a;
    input b;
    input select;
    output result;
```

If select is '1', b is selected, otherwise a is selected.

Complete the code, and test it using the provided mux\_tb.v testbench.

2. Half adder

Design a 1-bit half adder using structural gate level Verilog. The adder accepts two binary inputs: a and b, and computes their output sum and carry:

```
module halfadder(a,b,sum,carry);
    input a,b;
    output sum, carry;
```

The files halfadder.v and halfadder\_tb.v contain a partial implementation for the half adder and its testbench. Complete the code, verify that it's working well using the testbench. In addition to the log, submit a waveform screenshot showing correct operation.

3. Full adder

Design a 1-bit full adder taking three 1-bit inputs: a, b, and ci, and giving sum and co.

```
module fulladder( sum, co, a, b, ci);
    input  a, b, ci;
    output sum, co;
```

Write a testbench and use it to simulate the adder, checking all input combinations.

4. Four bit unsigned adder

Design a 4-bit unsigned adder using instantiation of four 1-bit adders.

```
module add4( sum, co, a, b, ci);
    input  [3:0] a, b;
    input  ci;
    output [3:0] sum;
    output co;
```

No need to write a testbench, since it will be tested as part of the next exercise.

### 5. Four bit add/sub unit

Use the 4-bit unsigned adder from the previous exercise to design a 4-bit signed add/sub unit, which can either add or sub based on a mode input (0 add, 1 sub).

```
module addsub( result, operand_a, operand_b, mode );
    input  [3:0] operand_a, operand_b;
    input  mode;
    output [3:0] result;
```

Test it with the provided testbench, and submit a wave screenshot of the simulation.

### 6. Parity

Design a state machine which will accept a stream of bits (one every clock), and will output '1' if the number of ones accepted so far is even, or '0' otherwise.

```
module iseven(clk, in, reset, out);
    input clk, in, reset;
    output out;
```

Fill in the provided parity.v and parity\_tb.v and submit them along with the Verilog log file.

### 7. Bi-Modal N-bit Saturating Counter

Design an N-bit saturating counter circuit, which is widely used for branch prediction. The circuit maintains an N-bit counter, initialized to 0 at reset=1. The counter value is preserved when reset=0 and branch=0, whereas it is updated when reset=0 and branch=1 according to the following rule:

$$\begin{aligned} \text{counter}(t+1) &= \min\{ \text{counter}(t) + 1, 2^N - 1 \} && \text{if } taken == 1 \\ \text{counter}(t+1) &= \max\{ \text{counter}(t) - 1, 0 \} && \text{if } taken == 0 \end{aligned}$$

The output *prediction* equals 1 if and only if  $\text{counter}(t) \geq 2^{(N-1)}$

```
module sat_count(clk, reset, branch, taken, prediction);
    parameter N=2;
    input clk, reset, branch, taken;
    output prediction;
```

Submit a state diagram of sat\_count(N=2). Fill the sat\_count.v code, and write a testbench sat\_count\_tb.v. Your test-bench must perform a test of sat\_count(N=2) and print a final answer such as "PASSED ALL TESTS".

### 8. fifo(N,W)

Design a first-in-first-out queue synchronous module which satisfies the specifications below:

```
module fifo(clk, reset, in, push, pop, out, full);
  parameter N=4; // determines the maximum number of words in queue.
  parameter M=2; // determines the bit-width of each word stored in the queue.

  input clk, reset, push, pop;
  input [M-1:0] in;
  output [M-1:0] out;
  output full;
```

The functionality:

Let  $W(t) = \langle w_1, w_2, \dots, w_n \rangle$  denote the words stored at the module at time  $t$ , where  $1, \dots, n$  corresponds to the chronological order of the words registered at the queue ( $n$  is the oldest). The outputs must respect the following behavior:

$full(t) = 1$  iff  $n=N$   
 $out(t) = w_n$  iff  $n>0$  (otherwise  $out(t)=0^M$ )  
 $W(t+1) = \langle \rangle$  (empty queue) iff  $reset(t)=1$   
If  $reset(t)=0$  then the functionality depends on  $n$ :

$n=0$ :

|                               |                                |
|-------------------------------|--------------------------------|
| $W(t+1) = \langle in \rangle$ | iff $push(t)=1$ and $pop(t)=*$ |
| $W(t+1) = W(t)$               | iff $push(t)=0$ and $pop(t)=*$ |

$0 < n < N$ :

|   |                                |
|---|--------------------------------|
| $W(t+1) = \langle in, w_1, w_2, \dots, w_{n-1} \rangle$ | iff $push(t)=1$ and $pop(t)=1$ |
| $W(t+1) = \langle in, w_1, w_2, \dots, w_n \rangle$     | iff $push(t)=1$ and $pop(t)=0$ |
| $W(t+1) = \langle w_1, w_2, \dots, w_{n-1} \rangle$     | iff $push(t)=0$ and $pop(t)=1$ |
| $W(t+1) = W(t)$   | iff $push(t)=0$ and $pop(t)=0$ |

$n=N$ :

|   |                                |
|---|--------------------------------|
| $W(t+1) = \langle in, w_1, w_2, \dots, w_{N-1} \rangle$ | iff $push(t)=1$ and $pop(t)=1$ |
| $W(t+1) = W(t)$   | iff $push(t)=*$ and $pop(t)=0$ |
| $W(t+1) = \langle w_1, w_2, \dots, w_{N-1} \rangle$     | iff $push(t)=0$ and $pop(t)=1$ |

Fill the `fifo.v` code, and write a testbench `fifo_tb.v` which instantiates `fifo(4,2)` module (set  $N, M$  to 4,2 from the test-bench using parameter overriding). Your test-bench must print a final answer such as "PASSED ALL TESTS".